

---

# Digital Logic Recap

ECSE 324: Computer Organization

Fall 2023 - Tutorial 1

Revision History: A. Karsidag (2025), J. Li (2023), M. Jalaledine (2022)

---

# Outline

- Boolean Algebra
- Combinational Circuits
- Sequential Circuits

# Boolean Algebra

- Operations: OR (+);  
AND ( $\times$ ) (omit  $\times$  for saving space);  
NOT ( $'$  or  $\bar{\phantom{x}}$ ).
- Laws: Commutative ( $a + b = b + a, ab = ba$ );  
Distributed ( $a \times (b + c) = ab + ac, a + bc = (a + b)(a + c)$ );  
Associative ( $a + (b + c) = (a + b) + c, a(bc) = (ab)c$ );  
Identity ( $a + 0 = a, a \times 1 = a$ );  
Complement ( $a + a' = 1, a \times a' = 0$ ).

# Boolean Algebra

- DeMorgan's Laws:  $(a + b + c + \dots)' = a' \times b' \times c' \dots$ ;  
 $(a \times b \times c \times \dots)' = a' + b' + c' + \dots$ .
- Sum of Product (SOP):  $(a \times b) + (c \times d)$ .
- Product of Sum (POS):  $(a + b) \times (c + d)$ .

# Boolean Algebra

- K-Map

cd \ ab	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	1	1	1	X
10	0	0	0	1

SOP

$$f = ca' + ab + cd'$$

POS

$$f = (a + c)(b + c)(a' + b + d')$$

# Boolean Algebra

cd \ ab	00	01	11	10
00	1	1	1	1
01	1			
11	1			
10	1			

Why SOP? Why POS?

Simplify the logical expression!

$$f = a'b'c'd' + a'b'c'd + a'b'cd + a'b'cd' + a'bc'd' + abc'd' + ab'c'd'$$



$$f = a'b' + c'd'$$

# Boolean Algebra

Q1

Simplify the following expression:

$$f = (a' + b' + c + d) \times (a' + b' + c + d') \times (a' + b' + c' + d') \times (a + b' + c' + d') \times (a + b + c' + d') \times (a + b + c' + d) \times (a + b' + c' + d) \times (a' + b + c' + d)$$

# Combinational Circuits

Logic gates:

NOT gate:  $y = x'$




AND gate:  $y = x_1 \times x_2$




OR gate:  $y = x_1 + x_2$



 $n$  inputs AND gates:  $y = x_1 \times x_2 \times \dots$



 
$n$  inputs OR gates:  $y = x_1 + x_2 + \dots$






# Combinational Circuits

$(x_1 + x_2) \times x_3$ :

 

$((x')')'$ :

 

---

# Combinational Circuits


Q2

What is the difference between a demultiplexer and a decoder?

# Combinational Circuits

 Q3


Design a combinational circuit for the following one-hot encoder:




x1	x2	x3	x4	f1	f2
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

# Sequential Circuits

Combinatorial vs Sequential:

 

 Combinational:  $y_i = f_i(x_1, \dots, x_n)$



Sequential: 1) Memory 2) Time Steps (Clock)

$$y_i^t = f_i(x_1^t, \dots, x_n^t, s_1^t, \dots, s_m^t)$$

$$s_i^{t+1} = g_i(x_1^t, \dots, x_n^t, s_1^t, \dots, s_m^t)$$

---

# Sequential Circuits

Q4

What is the difference between a latch and a flip-flop?



---

# Sequential Circuits

Q5 What is the difference between different designs (Mealy and Moore Machine) of a finite state machine (FSM)?

  
# Sequential Circuits

- The FSM (TFF) can be in one of two states
  - State A:  $Q = 0$
  - State B:  $Q = 1$
- Depending on the input, the FSM may change states at each positive edge of the clock
  - When  $w = 0$  the state does not change
  - When  $w = 1$  the state toggles
- The output  $z$  depends on the state only  $\rightarrow$  Moore FSM
- Initial state: the state at which the FSM “starts”



# State Diagram and Table

State diagram

 

State table

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	B	A	1



# Sequential Circuits

Q6

Write down a state transition diagram for a sequence detector that detects two consecutive bit 1s in the input data stream. 1 bit arrives at the input per clock cycle. For example, a bit 0 arrives at the clock period 1, a bit 1 arrives at the clock period 2, a bit 1 arrives at the clock period 3, and the detector outputs the signal for successfully detecting two consecutive bit 1s. If the next incoming bit is 1 once two consecutive bit 1s are detected, the detector still outputs the signal for successfully detecting two consecutive bit 1s.